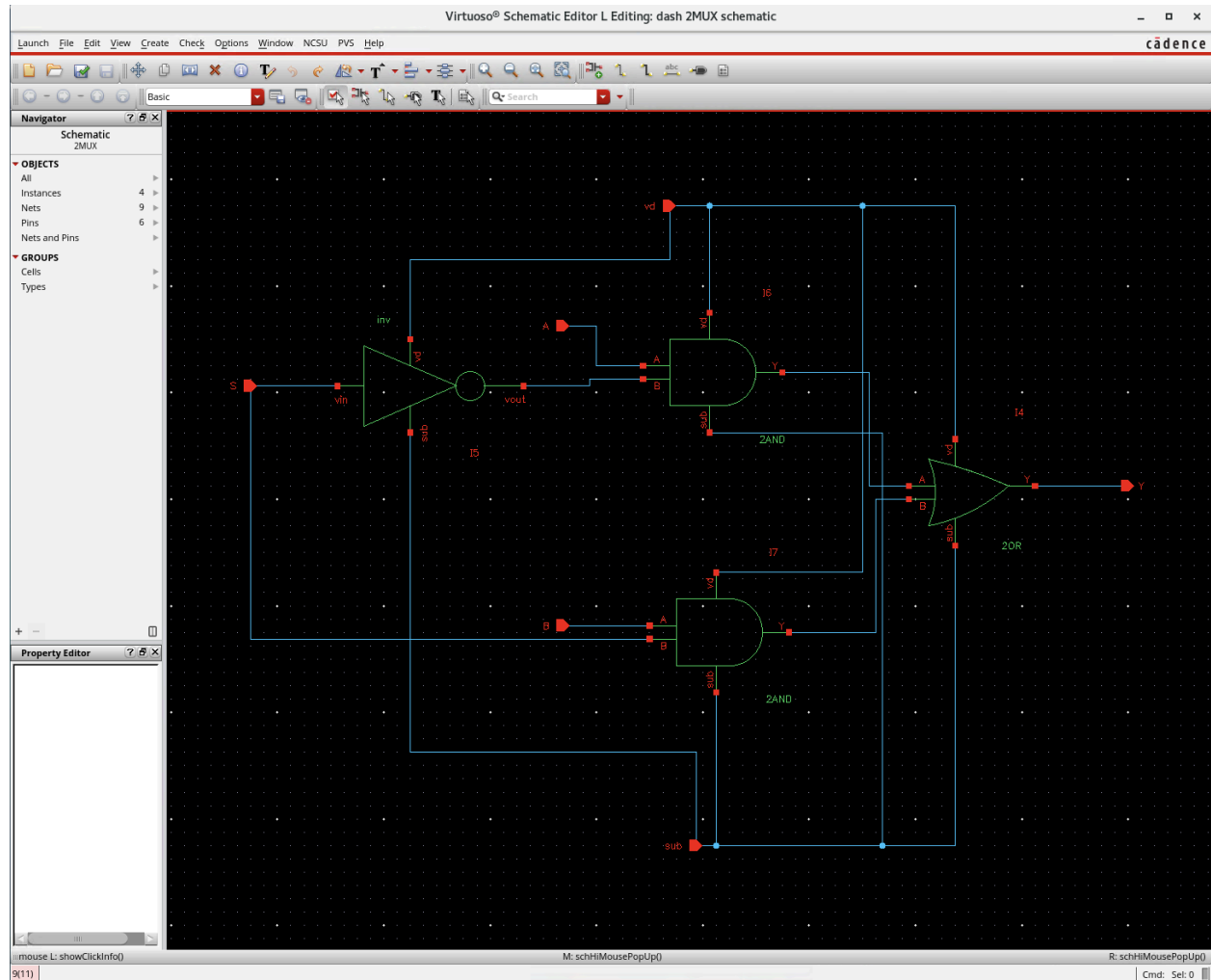



Project 1 Part 1

Schematic and simulation of a 2:1 MUX


Schematic of the 2:1 MUX



Schematic used to simulate the 2:1 MUX

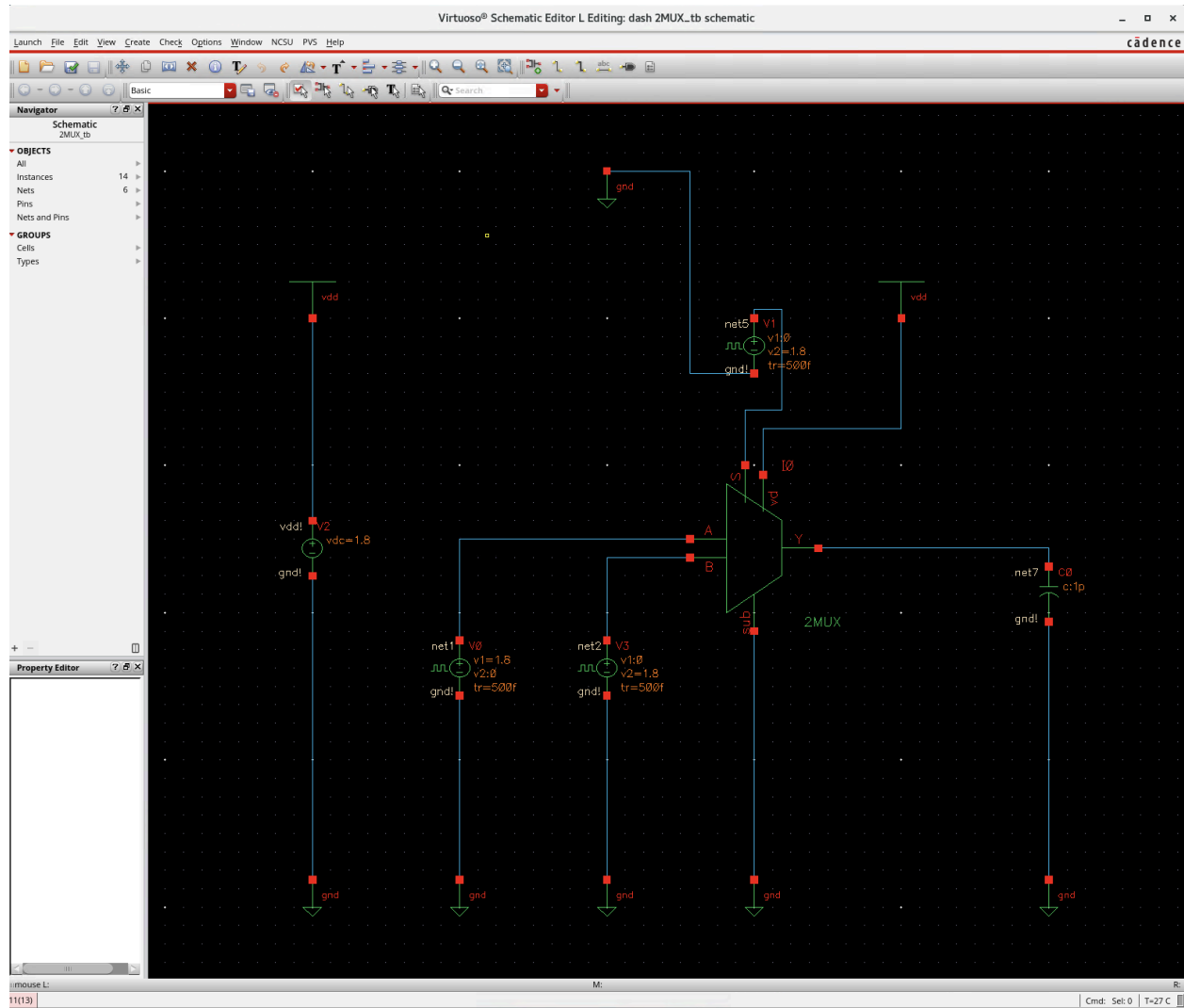

Simulation results

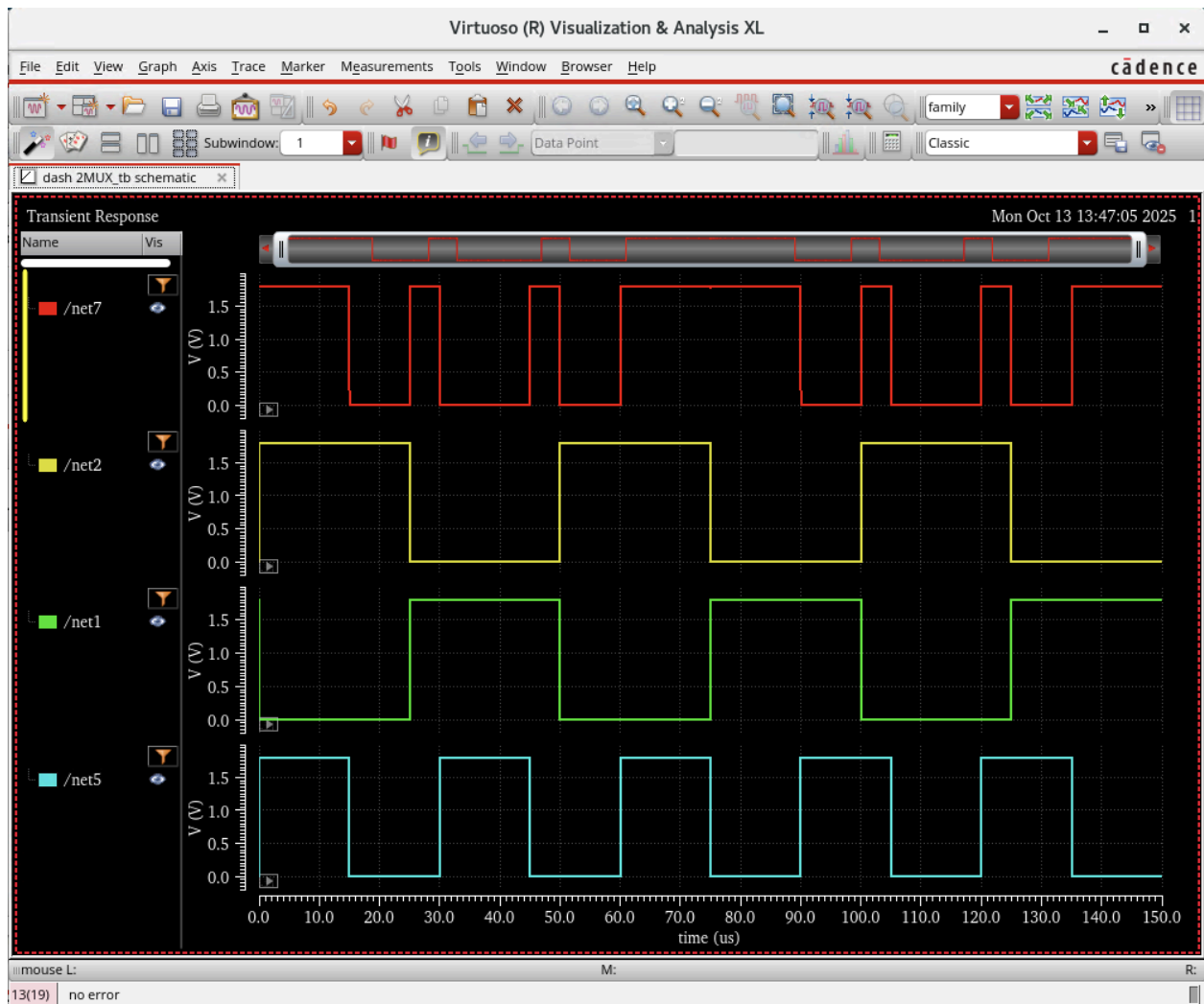

Net 7- Y (Vout)

Net 2- B (I2)

Net 1- A (I1)

Net 5- S