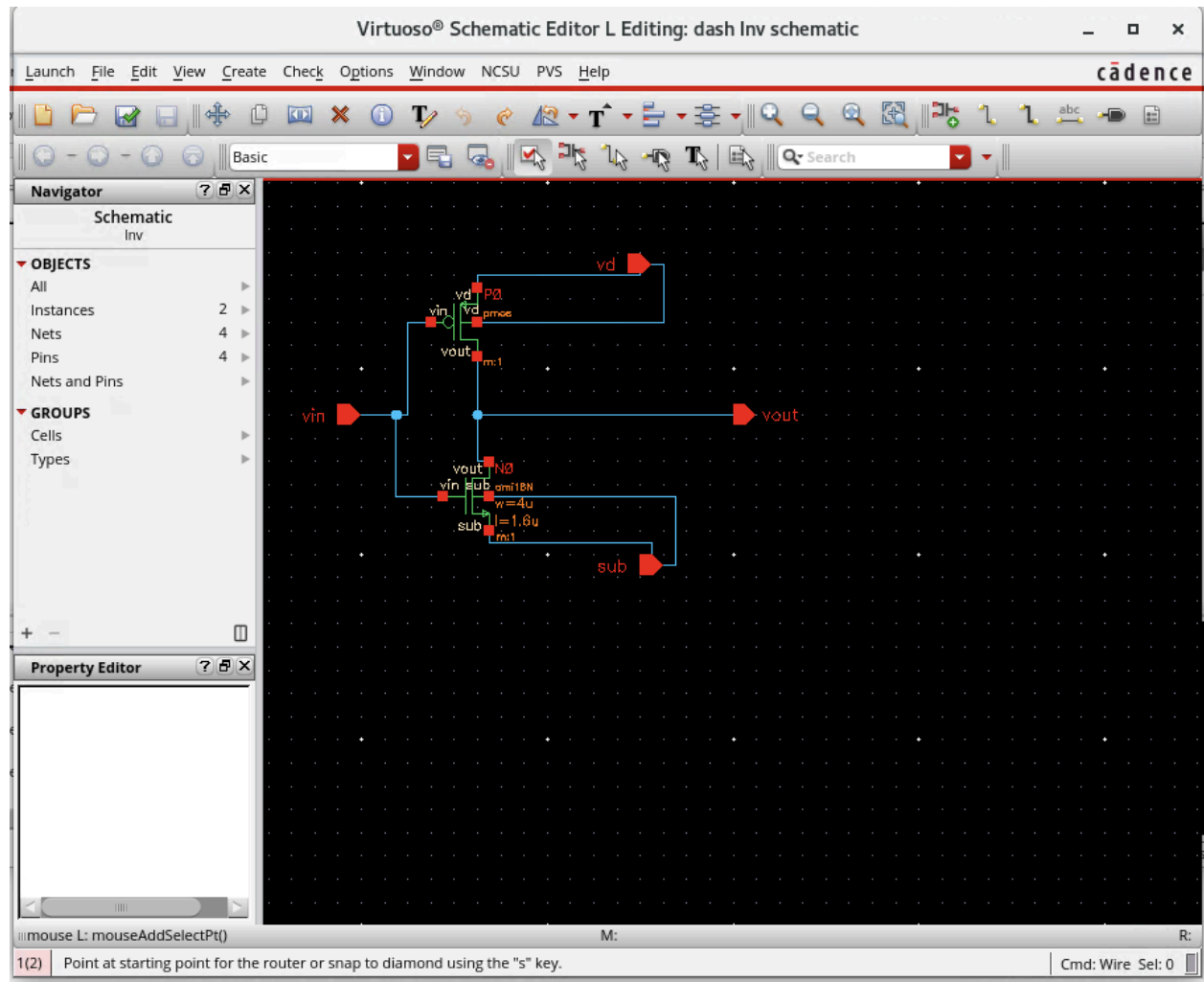


Lab 1- Inverter Tutorial

Schematic Creation



Symbol Creation

