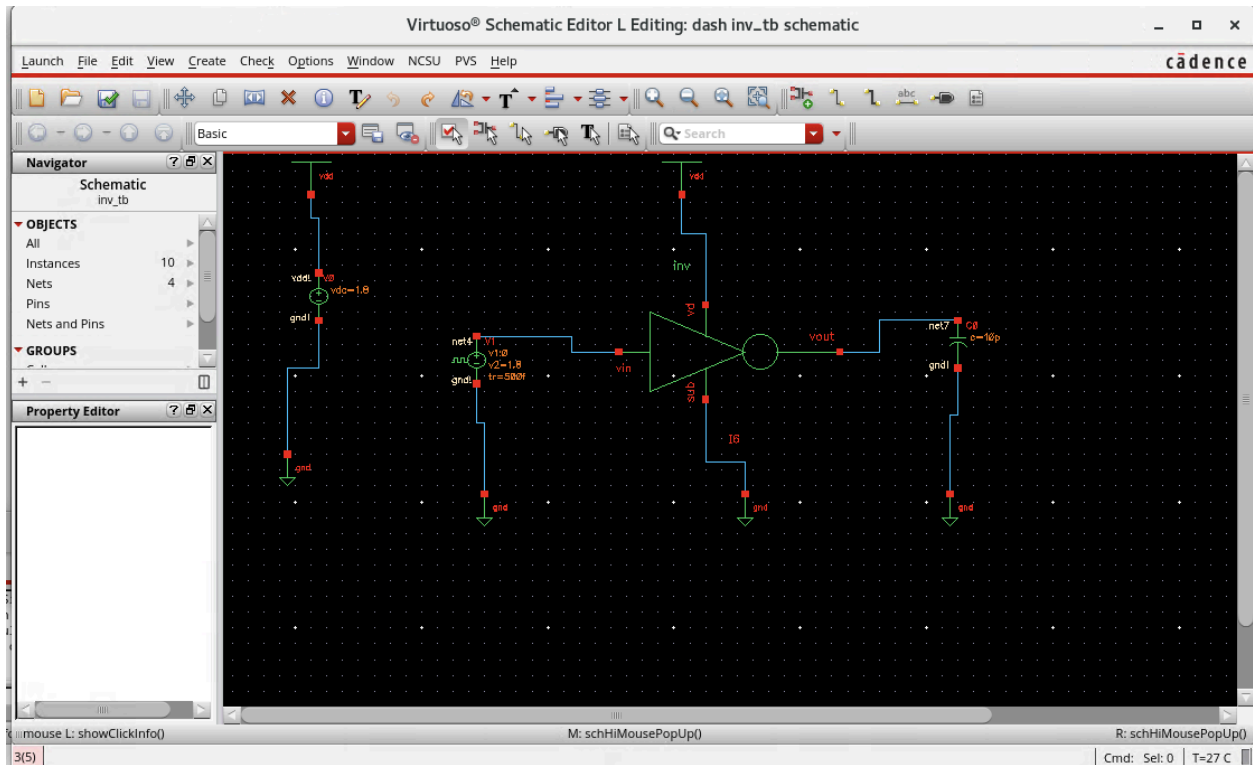


Lab2

Inverter Tutorial: Test Bench Creation and Transient Simulation

Schematic of your test bench



Simulation waveforms

